

- Use this schematic when there is only one turn-signal indicator on the dash instead of two
- Splice into turn-signal outputs on front POWERCELL
- Route back to the dash through 22-awg wire
- Use diodes to block one output from turning on the other
- Diodes can be purchased at Radio Shack, www.digikey.com or www.mouser.com.
- P/N: 1N4001

